

Assignment 2

Nov. 1, 2021

1 DIGITAL DESIGN THEORY

Q. 1

(a) Let $F_1 = \sum m_i$ and $F_2 = \sum m_j$, then $E = F_1 + F_2 = \sum m_i + \sum m_j = \sum(m_i + m_j)$, which is the sum of the minterms of F_1 and F_2 .

(b) Let $F_1 = \sum m_i$ and $F_2 = \sum m_j$, then $G = F_1 \cdot F_2 = \sum m_i \cdot \sum m_j = \sum_i \sum_j (m_i \cdot m_j)$, where $m_i \cdot m_j = \begin{cases} 0 (i \neq j) \\ 1 (i = j) \end{cases}$, in this case only the minterms where both in (say, common to) F_1 and F_2 , a.k.a. appear to have the same i and j can be i in G .

Q. 2

(a) $F(x, y, z) = \Pi(0, 1, 2, 4, 6)$

(b) $F(A, B, C, D) = \Sigma(0, 1, 2, 4, 6, 7, 9, 10, 13, 14)$

Q. 3

(a)

Converting to min/max-terms

$$\begin{aligned}
 (b' + d)(a' + b' + c)(a' + c) &= b'a'a' + b'a'c + b'b'a' + b'b'c + b'ca' + b'cc + \\
 &\quad da'a' + da'c + db'a' + db'c + dca' + dcc \\
 &= a'b' + a'b'c + a'b' + b'c + a'b'c + b'c + a'd + a'cd + a'b'd + b'cd + a'cd + cd \\
 &= a'b' + a'b'c + b'c + a'd + a'cd + a'b'd + b'cd + cd \\
 &= a'b' + b'c + a'd + a'b'd + cd \\
 &= a'b' + b'c + a'd + cd
 \end{aligned}$$

Using K-map

		<i>cd</i>			
		00	01	11	10
<i>ab</i>	00				
	01	0			0
	11	0	0		0
	10	0	0		

$$(b' + d)(a' + b' + c)(a' + c) = a'b' + cd + a'd + b'c$$

(b)

$$\begin{aligned}
 xy + x'z' + x'yz &= xy(z + z') + x'(y + y')z' + x'yz \\
 &= xyz + xyz' + x'yz' + x'y'z' + x'yz \\
 &= \Sigma(0, 2, 3, 6, 7) \\
 &= \Pi(1, 4, 5) \\
 &= (x + y + z')(x' + y + z)(x' + y + z')
 \end{aligned}$$

Q. 4

(a)

$$\begin{aligned}
 y'z' + yz' + x'z &= (y' + y)z' + x'z && \text{(LHS)} \\
 &= z' + x'z \\
 &= x' + z' \\
 x' + xz' &= x' + z' && \text{(RHS)}
 \end{aligned}$$

Thus LHS = RHS, the equation is true.

(b)

$$\begin{aligned}
 x'y + xz + y'z' &= x'y(z + z') + x(y + y')z + (x + x')y'z' && \text{(LHS)} \\
 &= x'yz + x'yz' + xyz + xy'z + xy'z' + x'y'z' \\
 &= (xy'z + xy'z') + (x'yz' + x'y'z') + (x'yz + xyz) \\
 &= xy' + x'z' + yz && \text{(RHS)}
 \end{aligned}$$

Thus LHS = RHS, the equation is true.

Q. 5

(a)

		<i>yz</i>			
		00	01	11	10
<i>wx</i>	00				
	01				
	11	1	1		1
	10	1			1

$$F(w, x, y, z) = (wy'z' + wyz') + wx y' = wz' + wx y'$$

(b)

		<i>CD</i>			
		00	01	11	10
<i>AB</i>	00	1			1
	01		1	1	
	11		1	1	
	10	1			1

$$F(A, B, C, D) = BD + B'D'$$

(c)

		<i>CD</i>			
		00	01	11	10
<i>AB</i>	00				
	01			1	
	11	1	1	1	
	10	1	1	1	

$$AB'CD + AD + AC' + BCD = AC' + AD + BCD$$

(d)

		CD			
		00	01	11	10
AB	00		1		
	01	1	1		
	11			1	
	10		1	1	1


$$A'B'C'D + ABCD + A'BC' + AB'C + AB'D = A'BC' + B'C'D + ACD + AB'C$$

Q. 6


(a)

		CD			
		00	01	11	10
AB	00	0		0	
	01	0	0	0	
	11	0		0	
	10	0		0	
 
$$F(A, B, C, D) = (C + D)(C' + D')(A + B' + C)$$




or

 

(b)

		CD			
		00	01	11	10
AB	00				
	01				
	11				
	10	0	0		

$$F(A, B, C, D) = A' + B + C$$

 

Q. 7

(a)

		CD			
		00	01	11	10
AB	00	d	0	0	1
	01	1	0	1	d
	11	1	0	0	0
	10	d	0	0	1

$$F(A, B, C, D) = C'D' + B'D' + A'BC$$

$$= \Sigma(0, 2, 4, 6, 7, 8, 10, 12)$$

(b)

		CD			
		00	01	11	10
AB	00	d	d	0	1
	01	1	d	0	0
	11	1	0	0	1
	10	d	0	0	1

$$F(A, B, C, D) = B'D' + C'D' + AD'$$

$$= \Sigma(0, 2, 4, 8, 10, 12, 14)$$


Q. 8

$$F = A'BC'D + AB'CD' + ABC'D' + A'B'CD$$

$$= (A'D + AD')BC' + (AD' + A'D)B'C$$

$$= (A'D + AD')(BC' + B'C)$$

$$= (A \oplus D)(B \oplus C)$$

 

2 DIGITAL DESIGN LAB

2.1 Task 1

```
1 `timescale 1ns / 1ps
2
3 module seg_tube (
4     input [3:0] id,
5     output reg [7:0] seg_out
6 );
7     always @* begin
8         case(id)
9             0: seg_out=8'b1100_0000; // 0
10            1: seg_out=8'b1111_1001; // 1
11            2: seg_out=8'b1010_0100; // 2
12            3: seg_out=8'b1011_0000; // 3
13            default: seg_out = 8'b1111_1111; // off
14        endcase
15    end
16 endmodule
17
18 module enc (
19     input [3:0] bell,
20     input hi_fst,
21     output [7:0] seg_out, seg_en
22 );
23     assign seg_en = 8'b1111_1110;
24     reg [3:0] dispid;
25     always @* begin
26         case(hi_fst)
27             1: begin
28                 casex(bell)
29                     'b0000: dispid <= 'b100; // invalid flag
30                     'b0001: dispid <= 0;
31                     'b001x: dispid <= 1;
32                     'b01xx: dispid <= 2;
33                     'b1xxx: dispid <= 3;
34                 endcase
35             end
36             0: begin
37                 casex(bell)
38                     'b0000: dispid <= 'b100;
39                     'b1000: dispid <= 3;
40                     'bx100: dispid <= 2;
41                     'bxx10: dispid <= 1;
42                     'bxxx1: dispid <= 0;
43                 endcase
44             end
45         endcase
46     end
```

```

47     seg_tube st(.id(dispid), .seg_out(seg_out));
48 endmodule

```

The design file contains two module, the assistant module that helps converting an input id into the seg-tube-code, while the main module *mux* takes a priority switch and the input switches, then select the one having the highest priority and convert it into seg-tube-code. To make it elegant (that can use the assistant module *seg_tube*), though the code of wards 0 - 3 can be represented in a 2-bit binary number, I use a 3-bit register that can represent the no-switch-state. (say, *dispid* actually acts as

{disable_output, id[1], id[0]}

, this is only for convenience.)

```

1  # seg_tube
2  set_property IOSTANDARD LVCMOS33 [get_ports {seg_en[0]}]
3  set_property IOSTANDARD LVCMOS33 [get_ports {seg_en[1]}]
4  set_property IOSTANDARD LVCMOS33 [get_ports {seg_en[2]}]
5  set_property IOSTANDARD LVCMOS33 [get_ports {seg_en[3]}]
6  set_property IOSTANDARD LVCMOS33 [get_ports {seg_en[4]}]
7  set_property IOSTANDARD LVCMOS33 [get_ports {seg_en[5]}]
8  set_property IOSTANDARD LVCMOS33 [get_ports {seg_en[6]}]
9  set_property IOSTANDARD LVCMOS33 [get_ports {seg_en[7]}]
10 set_property IOSTANDARD LVCMOS33 [get_ports {seg_out[0]}]
11 set_property IOSTANDARD LVCMOS33 [get_ports {seg_out[1]}]
12 set_property IOSTANDARD LVCMOS33 [get_ports {seg_out[2]}]
13 set_property IOSTANDARD LVCMOS33 [get_ports {seg_out[3]}]
14 set_property IOSTANDARD LVCMOS33 [get_ports {seg_out[4]}]
15 set_property IOSTANDARD LVCMOS33 [get_ports {seg_out[5]}]
16 set_property IOSTANDARD LVCMOS33 [get_ports {seg_out[6]}]
17 set_property IOSTANDARD LVCMOS33 [get_ports {seg_out[7]}]
18 set_property PACKAGE_PIN A18 [get_ports {seg_en[7]}]
19 set_property PACKAGE_PIN A20 [get_ports {seg_en[6]}]
20 set_property PACKAGE_PIN B20 [get_ports {seg_en[5]}]
21 set_property PACKAGE_PIN E18 [get_ports {seg_en[4]}]
22 set_property PACKAGE_PIN F18 [get_ports {seg_en[3]}]
23 set_property PACKAGE_PIN D19 [get_ports {seg_en[2]}]
24 set_property PACKAGE_PIN E19 [get_ports {seg_en[1]}]
25 set_property PACKAGE_PIN C19 [get_ports {seg_en[0]}]
26 set_property PACKAGE_PIN E13 [get_ports {seg_out[7]}]
27 set_property PACKAGE_PIN C15 [get_ports {seg_out[6]}]
28 set_property PACKAGE_PIN C14 [get_ports {seg_out[5]}]
29 set_property PACKAGE_PIN E17 [get_ports {seg_out[4]}]
30 set_property PACKAGE_PIN F16 [get_ports {seg_out[3]}]
31 set_property PACKAGE_PIN F14 [get_ports {seg_out[2]}]
32 set_property PACKAGE_PIN F13 [get_ports {seg_out[1]}]
33 set_property PACKAGE_PIN F15 [get_ports {seg_out[0]}]
34
35 # priority/bell switches
36 set_property IOSTANDARD LVCMOS33 [get_ports {bell[0]}]
37 set_property IOSTANDARD LVCMOS33 [get_ports {bell[1]}]

```



```
38 set_property IOSTANDARD LVCMOS33 [get_ports {bell[2]}]
39 set_property IOSTANDARD LVCMOS33 [get_ports {bell[3]}]
40 set_property PACKAGE_PIN T5 [get_ports {bell[3]}]
41 set_property PACKAGE_PIN T4 [get_ports {bell[2]}]
42 set_property PACKAGE_PIN R4 [get_ports {bell[1]}]
43 set_property PACKAGE_PIN W4 [get_ports {bell[0]}]
44 set_property IOSTANDARD LVCMOS33 [get_ports hi_fst]
45 set_property PACKAGE_PIN U5 [get_ports hi_fst]
46 set_property DRIVE 12 [get_ports {seg_en[7]}]
47 set_property DRIVE 12 [get_ports {seg_en[6]}]
48 set_property DRIVE 12 [get_ports {seg_en[5]}]
49 set_property DRIVE 12 [get_ports {seg_en[4]}]
50 set_property DRIVE 12 [get_ports {seg_en[3]}]
51 set_property DRIVE 12 [get_ports {seg_en[2]}]
52 set_property DRIVE 12 [get_ports {seg_en[1]}]
53 set_property DRIVE 12 [get_ports {seg_en[0]}]
```

Here we set the right-most 4 switches as the wards' bell input, and the 5th switch as the priority switch.



(a) When no ward press the bell, display nothing



(b) Showing in both high/low-first mode, when only one ward calls, display the corresponding room number



(c) Showing in high-first mode, bell 0&2 on → display 2; bell 0&1&2&3 on → display 3



(d) Showing in low-first mode, bell 1&3 on → display 1; bell 0&1&2&3 on → display 0

Figure 1: Verifying Task 1

2.2 Task 2

a	b	c	$F(a, b, c) = a \oplus b \oplus c$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

	ab			
	00	01	11	10
c 0		1		1
1	1		1	

$$F(a, b, c) = a'b'c + a'bc' + abc + ab'c' \quad (\text{SOP})$$

$$= (a + b + c)(a + b' + c')(a' + b' + c)(a' + b + c') \quad (\text{POS})$$

Design file

```

1  `timescale 1ns/1ps
2
3  module task2 (
4      input a, b, c,
5      output sop, pos
6  );
7      assign sop = ~a & ~b & c | ~a & b & ~c | a & b & c | a & ~b & ~c;
8      assign pos = (a | b | c) & (a | ~b | ~c) & (~a | ~b | c) & (~a | b | ~c);
9  endmodule

```

Simulation file

```


1  `timescale 1ns/1ps
2
3  module tsk2tb ();
4      reg a, b, c;
5      wire sop, pos;
6
7      task2 t(a, b, c, sop, pos);

```

```

8
9   initial begin
10       {a, b, c} = 3'b000;
11       while ({a, b, c} < 3'b111)
12           #10 {a, b, c} = {a, b, c} + 1;
13       #10 $finish();
14   end
15 endmodule

```

 

From the waveform above we see:

- ① The truth-values of SOP and POS design are always the same.
- ② When the number of *true* in the three variables a, b, c is odd, the truth value of $a \oplus b \oplus c$ is *true*, otherwise is *false*. The result keeps the same as the truth table.

2.3 Problems & Solutions

- (1) At first I directly used part of the constraint file (about the seg-tube) provided on the lab scission, then I found there always light up two numbers together. After checking the design file, constraint file and the minisys user manual carefully, I found there's a mis-constrained port and fixed it.
- (2) Designing the seg-tubes that are low-level effective is no that intuitive and need much care. An intuitive way is designing them in high-level way that use 1 to active one, and add a *bitwise not* to transverse them.
- (3) Maybe the next assignment could be harder and contains more questions :)